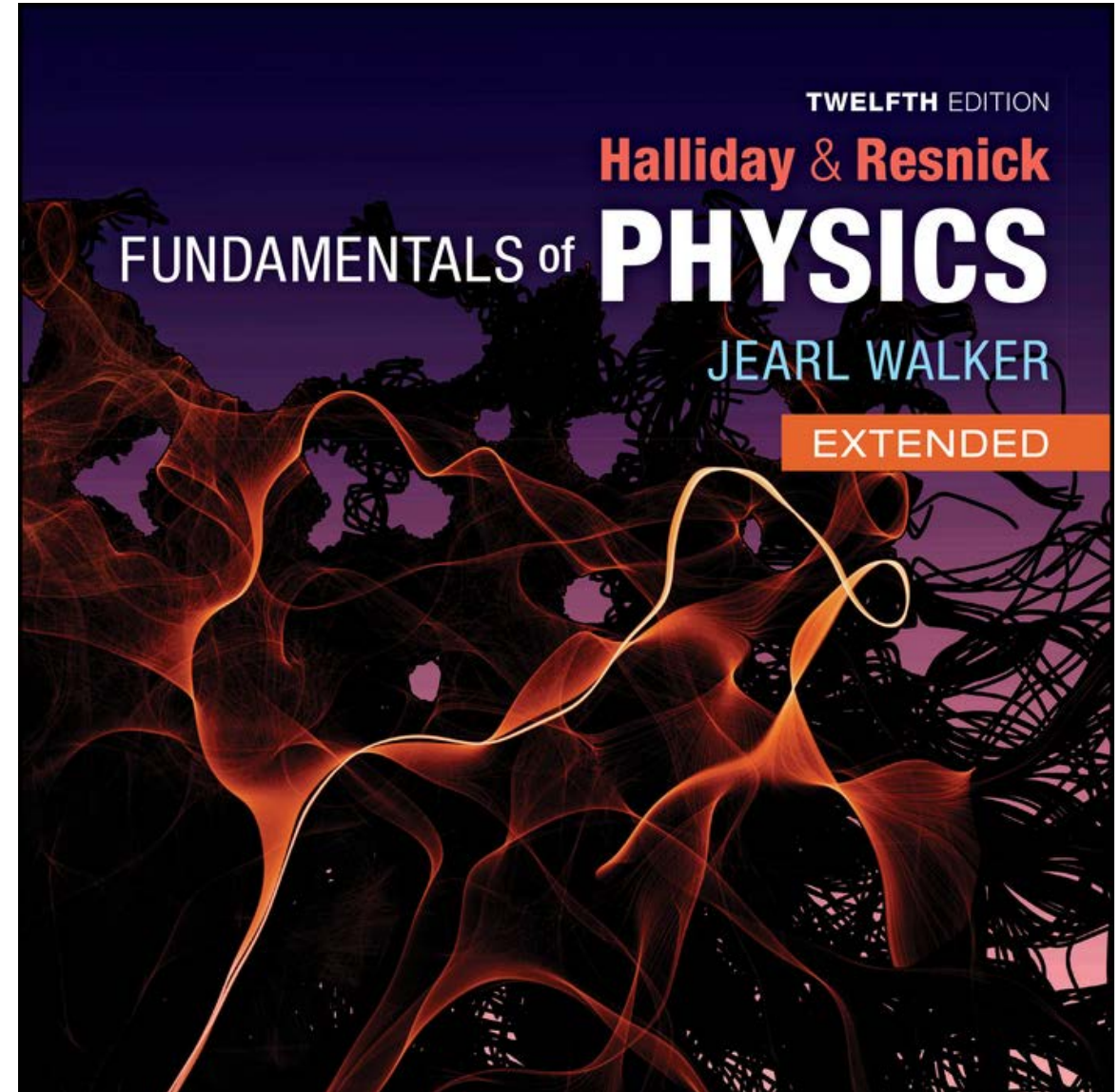


Fundamentals of Physics, Twelfth Edition. Halliday & Resnick, Walker

Chapter 25

Capacitance



Chapter 25

Capacitance

- min 4-5 grades
- more than 10 marks on Kirchoff's law

- 25.1 Capacitance
- 25.2 Calculating the Capacitance
- 25.3 Capacitors in Parallel and in Series
- 25.4 Energy Stored in an Electric field
- 25.5 Capacitors with a Dielectric

capacitor: store charge and energy
(device)

lamps/TV/charger

2 aluminum foil → store charge/energy
(conducting plates)
between insulator: dielectric → before it was air/vacuum
when inserted can make as thin as possible

spherical
cylindrical:
parallel-plate:

Section 25.1 Capacitance

Capacitance: Definition


A capacitor consists of two isolated conductors (the plates) with charges $+q$ and $-q$. Its **capacitance** C is defined from

$$q = CV.$$

$$1 \text{ farad} = 1 \text{ F} = 1 \text{ coulomb per volt} = 1 \text{ C/V.}$$



Where :

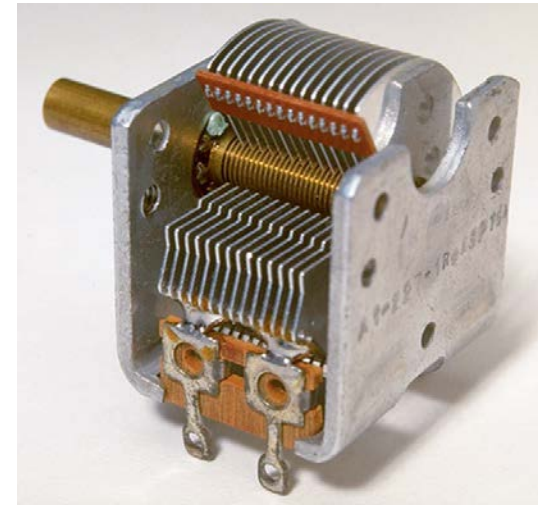- C : is the capacitance and it's always a positive quantity
- Q : is the charge on each plate
- V : is the potential difference between the two plates



Parallel Plate Capacitor

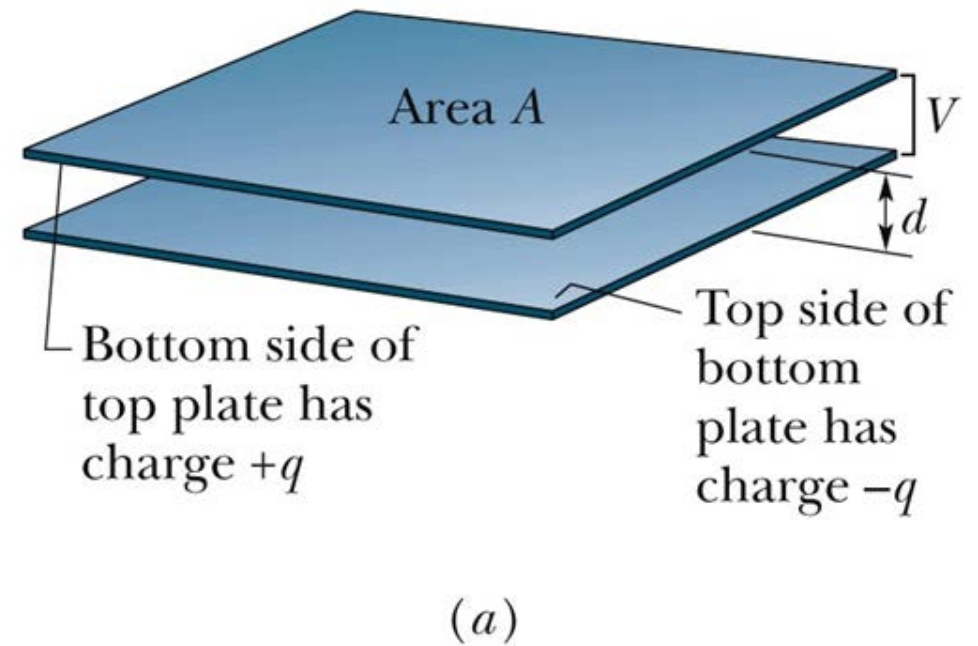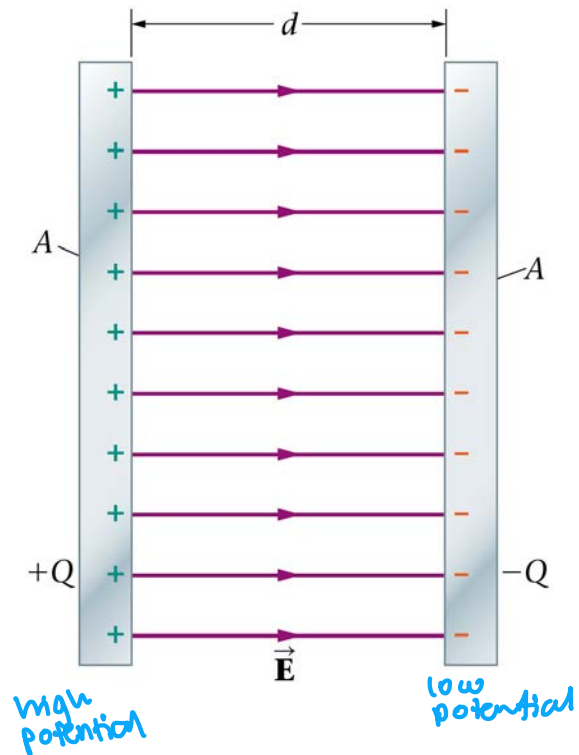A parallel-plate capacitor, made up of two plates of area A separated by a distance d . The charges on the facing plate surfaces have the same magnitude q but opposite signs





Charging a Capacitor


When a circuit with a battery, an open switch, and an uncharged capacitor is completed by closing the switch, conduction electrons shift, leaving the capacitor plates with opposite charges.

ohms law

capacitor symbol

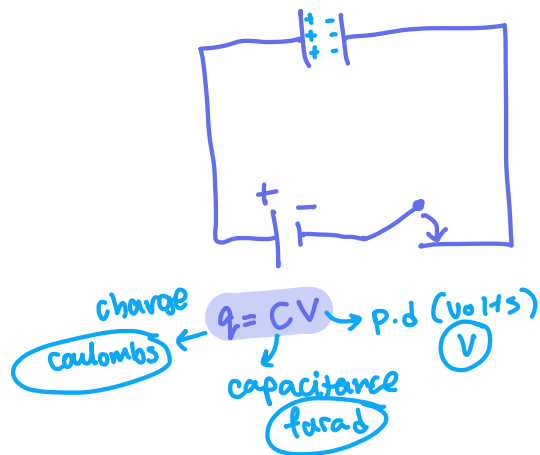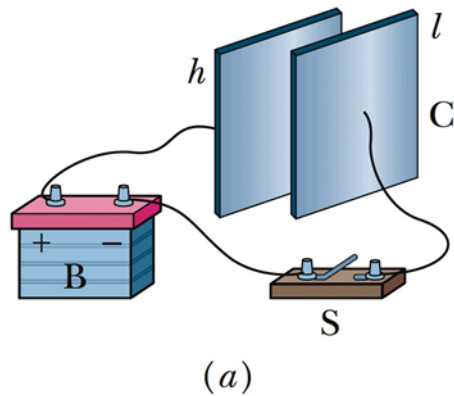

→ capacitor (fixed)

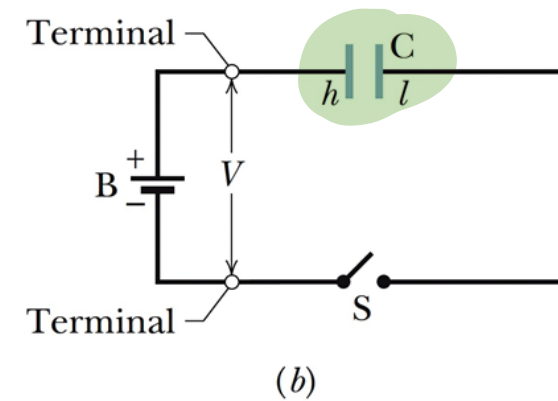

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

Fig. (a), a battery B, a switch S, an uncharged capacitor C, and interconnecting wires form a circuit. The same circuit is shown in the schematic diagram of Fig. (b), in which the symbols for a battery, a switch, and a capacitor represent those devices. The battery maintains potential difference V between its terminals. The terminal of higher potential is labeled + and is often called the positive terminal; the terminal of lower potential is labeled - and is often called the negative terminal.


Gauss' Law for Calculating Capacitance

To relate the electric field \vec{E} between the plates of a capacitor to the charge q on either plate, we shall use Gauss' law:


$$\epsilon_0 \oint \vec{E} \cdot d\vec{A} = q.$$

A Gaussian surface encloses the charge on the positive plate. The integration is taken along a path extending directly from the negative plate to the positive plate. We obtain :

$$q = \epsilon_0 EA$$

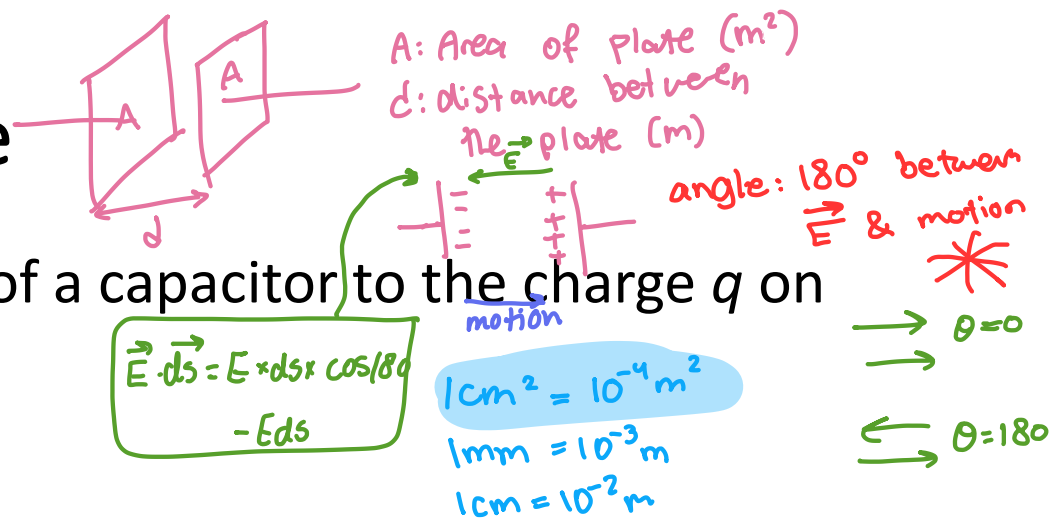

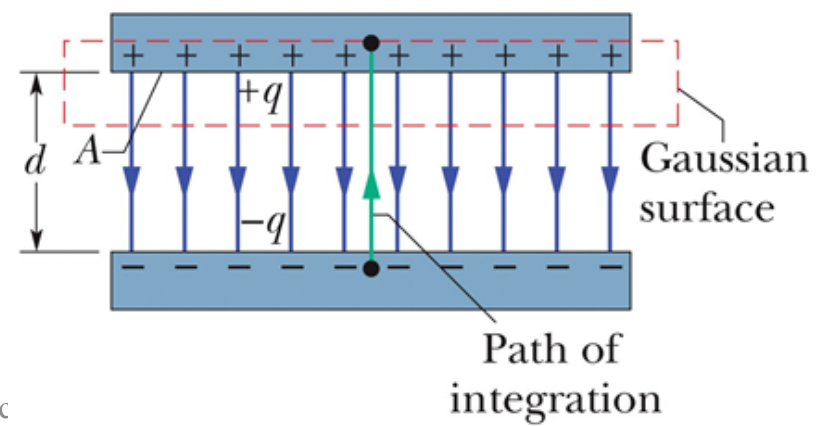We use Gauss' law to relate q and E . Then we integrate the E to get the potential difference.



➤ The potential difference between the plates of a capacitor is related to the field by:

going from - to +

$$V_f - V_i = - \int_i^f \vec{E} \cdot d\vec{s}$$

$\Phi = \frac{q}{\epsilon_0}$ (Gauss law) $\left\{ \begin{array}{l} EA = \frac{q}{\epsilon_0} \\ q = EA\epsilon_0 \end{array} \right\} \Delta V = V = V_f - V_i$
 $\int \vec{E} d\vec{A} = \frac{q}{\epsilon_0}$

➤ Letting V represent the difference $V = V_f - V_i$, we can then recast the above equation as :

$$V = \int_-^+ E ds = E \int_0^d ds = Ed.$$

slide above * $\cos(180) = -1$ -ve cancel each other so we got +Ed

$$q = CV$$


$$\cancel{EA\epsilon_0} = \cancel{C}Ed$$

$$C = \frac{A\epsilon_0}{d}$$

➤ For this path, the vectors \vec{E} and $d\vec{s}$ will have opposite directions ; so, the dot product will be $(-Eds)$.

➤ Now if we substitute $q = \epsilon_0 EA$ and $V = Ed$ into $q = CV$, we get,
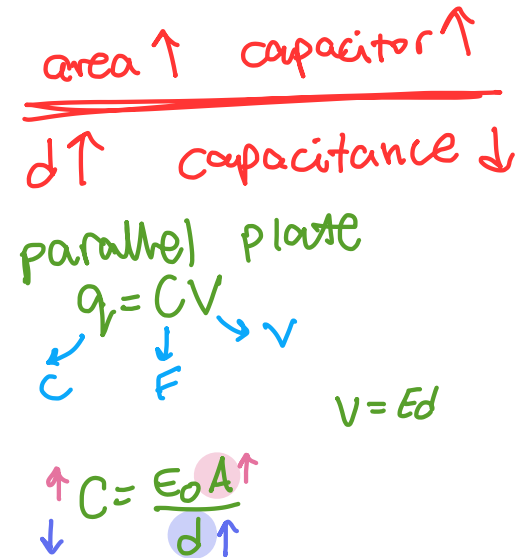
$$C = \frac{\epsilon_0 A}{d} \quad (\text{parallel-plate capacitor}).$$



Example

- A parallel plate capacitor is constructed with plates of area (0.028 m²) and separation (0.55 mm). $d = 0.55 \text{ mm} \times \frac{10^{-3} \text{ m}}{1 \text{ mm}} = 5.5 \times 10^{-4} \text{ m}$
 - Find the magnitude of the charge on each plate of this capacitor when the potential difference between the plates is (20.1 V) . $\rightarrow \checkmark$
 - What is the magnitude of the electric field between the plates of the capacitor.

Given: $A = 0.028 \text{ m}^2$
 $d = 5.5 \times 10^{-4} \text{ m}$
 $V = 20.1 \text{ V}$

Should know $\rightarrow \epsilon_0 = 8.85 \times 10^{-12}$

(a) $Q = CV$
 $= \frac{\epsilon_0 A}{d} V$
 $\frac{8.85 \times 10^{-12} (0.028)}{(5.5 \times 10^{-4})} (20.1) = 9.05 \times 10^{-9} \text{ C}$

(b) $E = \frac{V}{d} = \frac{20.1}{5.5 \times 10^{-4}} = 36545.45 \frac{\text{V}}{\text{m}}$

Section 25.3 Capacitors in Parallel and In Series


Net/Equivalent Capacitance for Capacitors in Parallel

When a potential difference V is applied across several capacitors connected in parallel, **that potential difference V is the same across each capacitor**. The total charge q stored on the capacitors is the sum of the charges stored on all the capacitors.


$$q_1 = C_1V, \quad q_2 = C_2V, \quad \text{and} \quad q_3 = C_3V.$$

The total charge on the parallel combination is then:
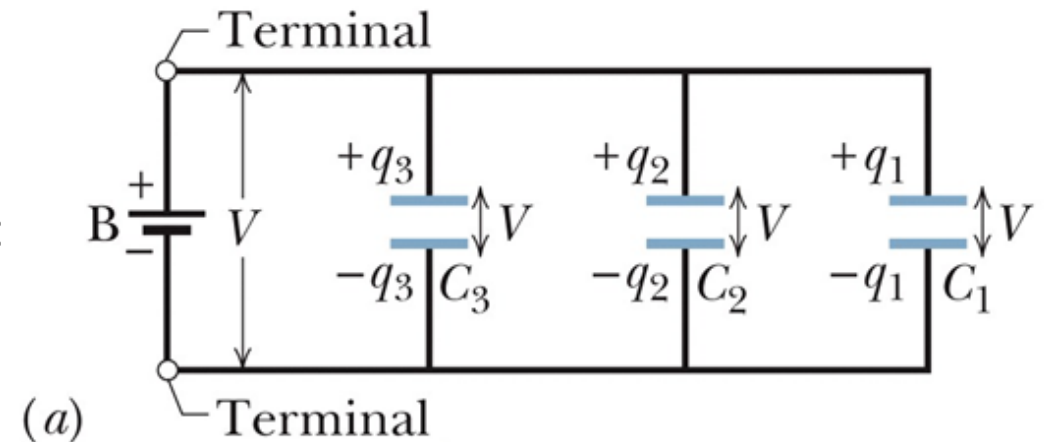
$$q = q_1 + q_2 + q_3 = (C_1 + C_2 + C_3)V.$$



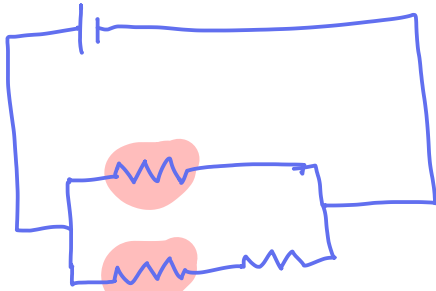Parallel capacitors and their equivalent have the same V (“par- V ”).



neither series nor parallel

Series: (same current / charge)
 parallel: (same potential difference / voltage)
 → same letters

not everytime split it's parallel X incorrect


letters won't be given
 I must know them

to X and ✓


doesn't change I: charges / time
 leaves and enter same

wire: letter don't change

anything else: change

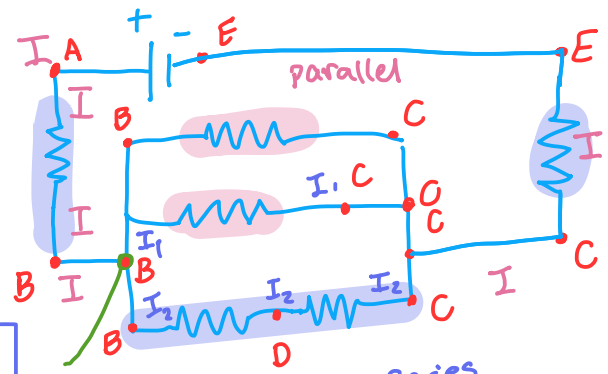

junction: where wires split

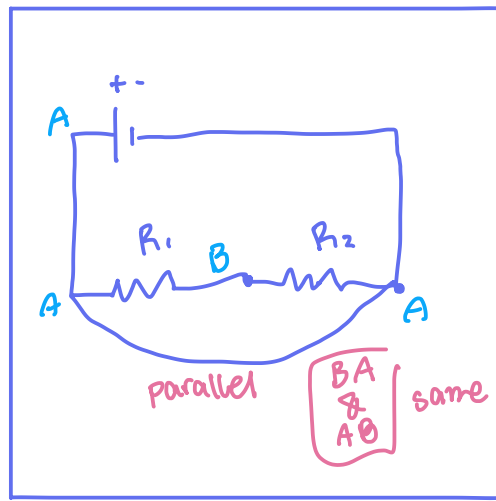


parallel
 BA & AB same

letter₁

letter₂ → to be parallel must have same

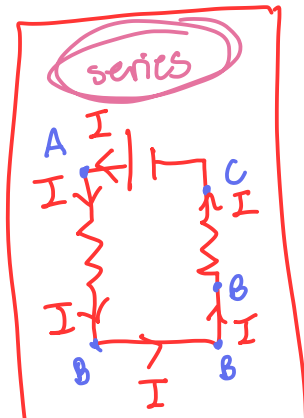current passing through / into / in
 p.d across / between



$$C = \frac{\epsilon_0 A}{d}$$

$\epsilon_0 \rightarrow \text{m}^2$
 $d \rightarrow \text{m}$


(air/vacuum)
plate capacitor

$$V = Ed$$



$$C_{eq} = CV$$

$F \rightarrow V$

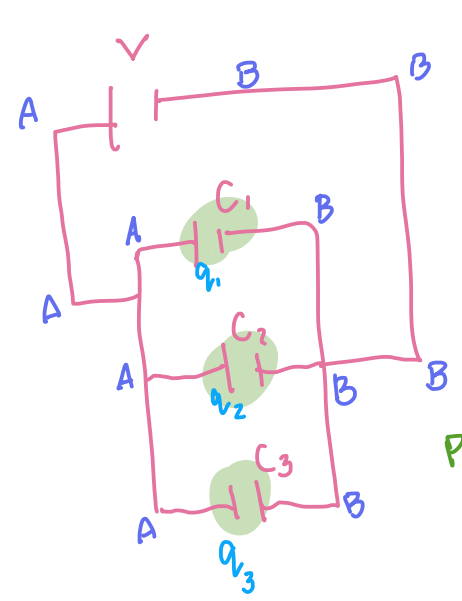


Farad prob wrong
pico nano } more accurate

$$\left. \begin{aligned} q_1 &= C_1 V_{AB} \\ q_2 &= C_2 V_{AB} \\ q_3 &= C_3 V_{AB} \end{aligned} \right\} \text{But } V_{AB} = V$$

$$q = C_{eq} V_{AB}$$


parallel

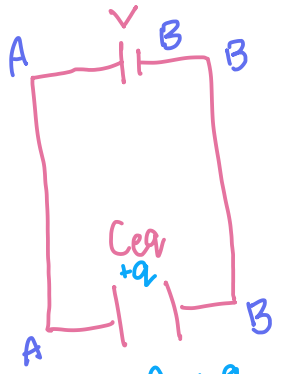

$$q = q_1 + q_2 + q_3$$

$$C_{eq} V_{AB} = C_1 V_{AB} + C_2 V_{AB} + C_3 V_{AB}$$

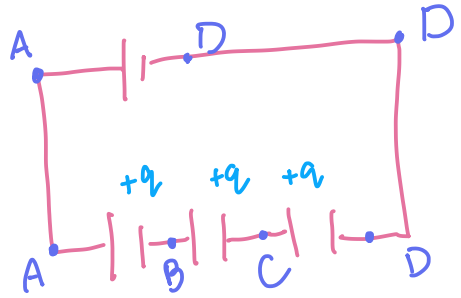
$$C_{eq} = C_1 + C_2 + C_3 \text{ parallel}$$



$$V_{AD} = V_{AB} + V_{BC} + V_{CD}$$

$$\frac{q}{C_{eq}} = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3}$$
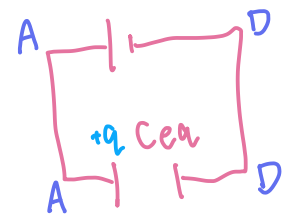
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



$$C_{eq}^{-1} = C_1^{-1} + C_2^{-1} + C_3^{-1}$$

The equivalent capacitance, with the same total charge q and applied potential difference V as the combination, is then

$$C_{\text{eq}} = \frac{q}{V} = C_1 + C_2 + C_3,$$

a result that we can easily extend to any number n of capacitors, as

$$C_{\text{eq}} = \sum_{j=1}^n C_j \quad (n \text{ capacitors in parallel}).$$


Net/Equivalent Capacitance for Capacitors in Series

When a potential difference V is applied across several capacitors connected in series, **the capacitors have same charge q** . The sum of the potential differences across all the capacitors is equal to the applied potential difference V .


$$V_1 = \frac{q}{C_1}, \quad V_2 = \frac{q}{C_2}, \quad \text{and} \quad V_3 = \frac{q}{C_3}.$$

The total potential difference V due to the battery is the sum:
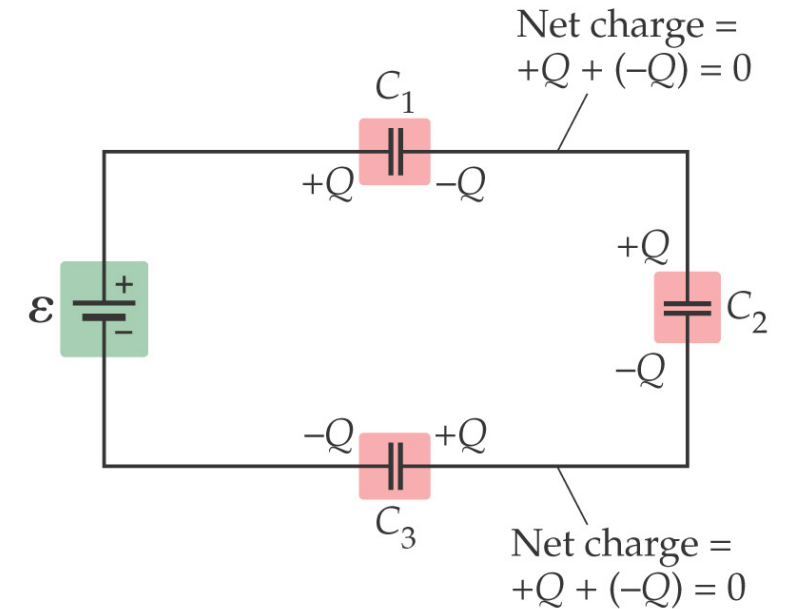
$$V = V_1 + V_2 + V_3 = q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right).$$



(a)

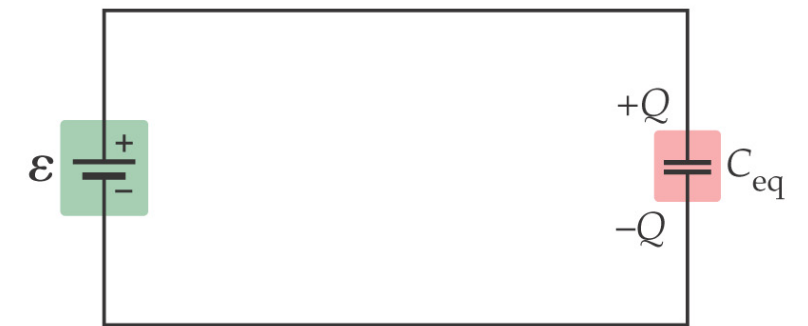

(b)

The equivalent capacitance is then:

$$C_{\text{eq}} = \frac{q}{V} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}},$$

or

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}.$$

$$\frac{1}{C_{\text{eq}}} = \sum_{j=1}^n \frac{1}{C_j} \quad (n \text{ capacitors in series}).$$

$$m = \times 10^{-3}$$

$$\mu = \times 10^{-6}$$

$$n = \times 10^{-9}$$

$$p = \times 10^{-12}$$

$$C_{eq} = \frac{q}{V}$$

Steps: must work backwards

① letters / label C_1, C_2

② Go from back, check relation

series: $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$
 parallel: $C_{eq} = C_1 + C_2$

③ Merge them (letters)
 C_{eq_1} with next C

④ Repeat ...

technique in solving:
 backwards

Example

Find the equivalent capacitance of the shown circuit


Charge in capacitor

(a) C_{eq} ? $20 \mu F$

C_4 & C_5 : series

$$\frac{1}{C_{45}} = \frac{1}{C_4} + \frac{1}{C_5} = \frac{1}{20} + \frac{1}{5} = \frac{1}{4} \quad C_{45} = 4 \mu F$$



(b) q, C_1 ?

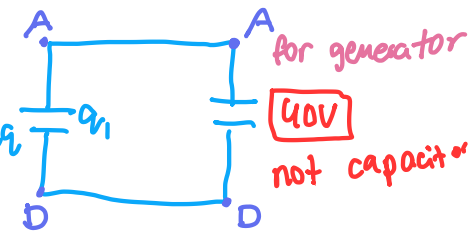


$$q_1 = C_{eq} \times V_{AD} = 20 \mu F \times 40V = 800 \mu C = 8 \times 10^{-4} C$$

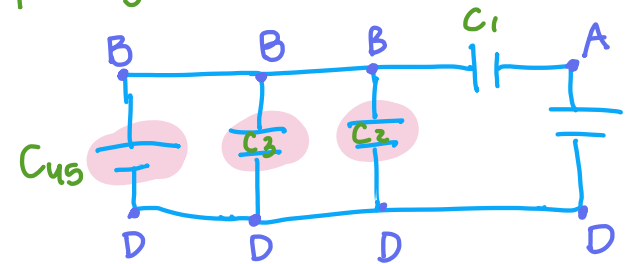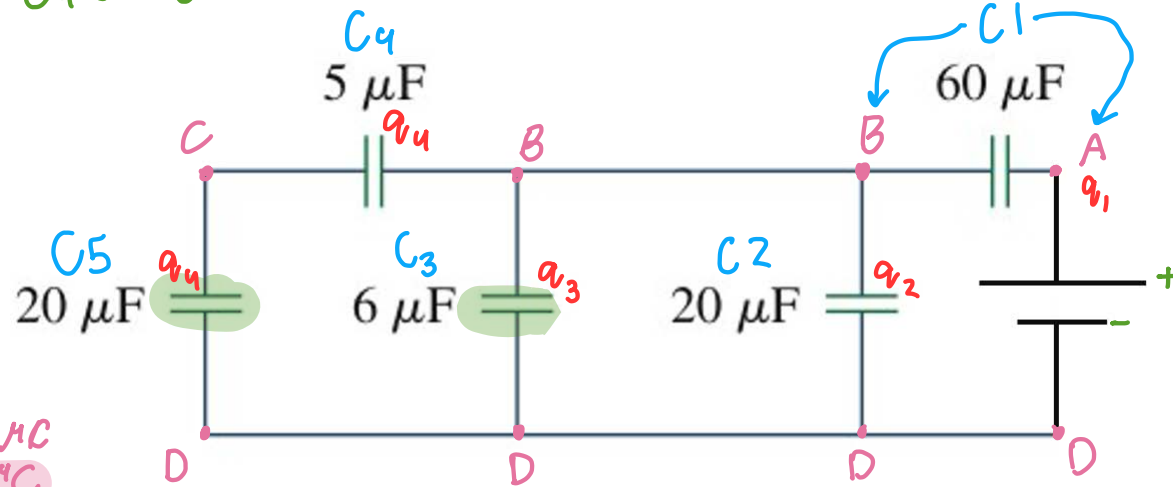(c) V, C_1

$$V_{C_1} = \frac{q_1}{C_1} = \frac{8 \times 10^{-4}}{60 \times 10^{-6}} V$$



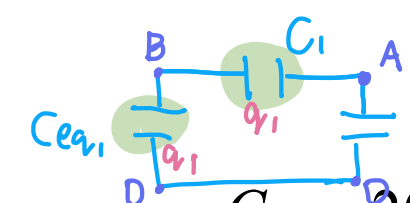C_2, C_3, C_4 in parallel
 $C_{eq_1} = 4 + 6 + 20 = 30 \mu F$



ans. $C_{eq} = 20 \mu F$ $C_{eq} = 20 \mu F$


$$\frac{1}{C_{eq_2}} = \frac{1}{C_1} + \frac{1}{C_{eq_1}} = \frac{1}{60} + \frac{1}{30}$$

Extra Practice

(a) Find the equivalent capacitance for the combination of capacitances shown in [Fig. 25.3.3a](#), across which potential difference V is applied. Assume

$$C_1 = 12.0 \mu\text{F}, \quad C_2 = 5.30 \mu\text{F}, \quad \text{and} \quad C_3 = 4.50 \mu\text{F}.$$

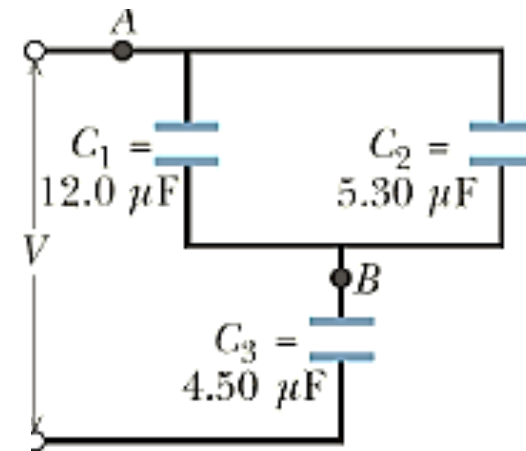
(b) The potential difference applied to the input terminals in [Fig. 25.3.3a](#) is $V = 12.5 \text{ V}$. What is the charge on C_1 ?



(a)


Solution:

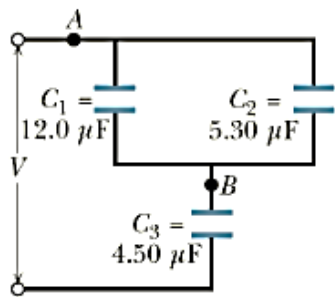We first reduce the circuit to a single capacitor.




(a)

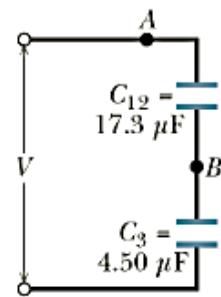The equivalent of parallel capacitors is larger.




(b)

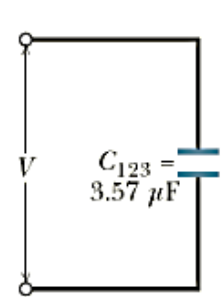The equivalent of series capacitors is smaller.




(c)

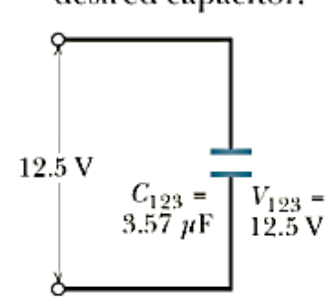Next, we work backwards to the desired capacitor.




(d)

Applying $q = CV$ yields the charge.

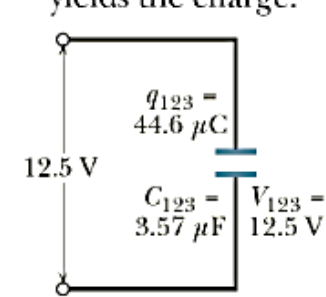


(e)

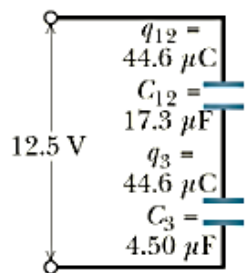Series capacitors and their equivalent have the same q ("seri- q ").




(f)

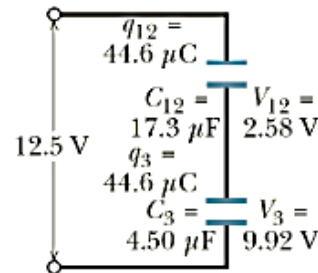Applying $V = q/C$ yields the potential difference.




(g)

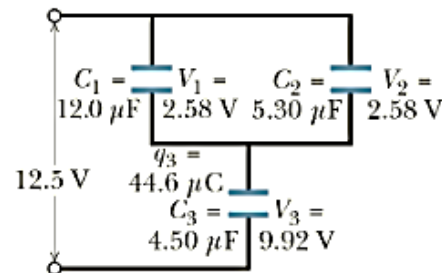Parallel capacitors and their equivalent have the same V ("par- V ").





(h)

Applying $q = CV$ yields the charge.


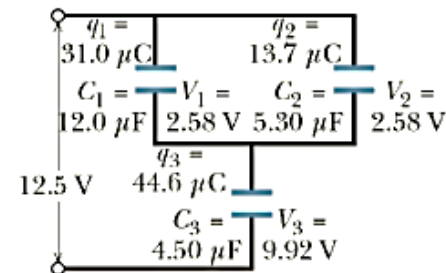


(i)

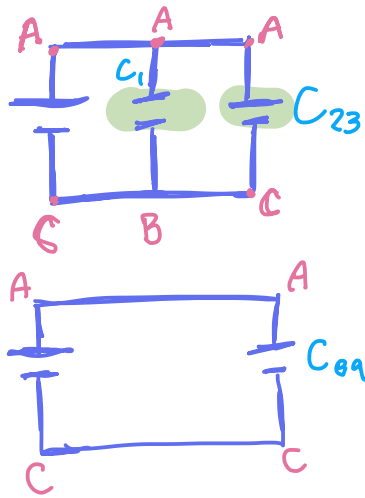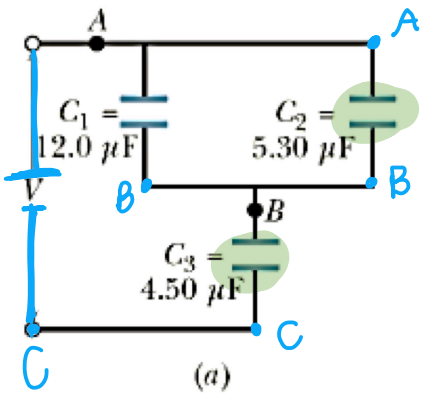

$$C_2 \text{ & } C_3 \text{ series} = \frac{1}{C_2} + \frac{1}{C_3} = 0.411 \text{ MF} = C_{23}$$
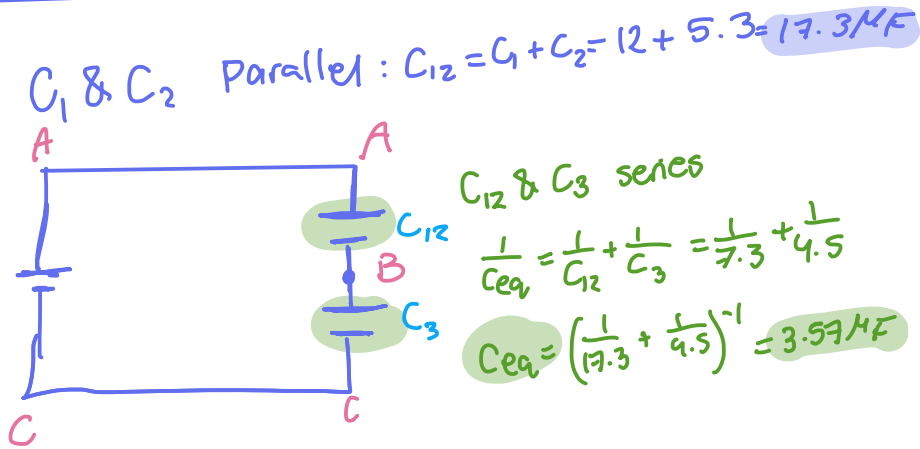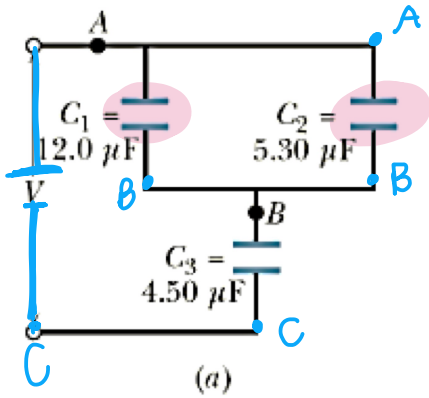
$$C_1 \text{ & } C_{23} \text{ series} = \frac{1}{C_{23}} + \frac{1}{C_1} = 2.516 \text{ MF} = C_{eq}$$




$$C_1 \text{ & } C_2 \text{ parallel: } C_{12} = C_1 + C_2 = 12 + 5.3 = 17.3 \text{ MF}$$




C_{12} & C_3 series

$$\frac{1}{C_{eq}} = \frac{1}{C_{12}} + \frac{1}{C_3} = \frac{1}{17.3} + \frac{1}{4.5}$$
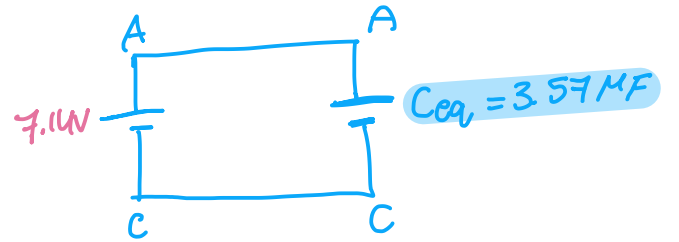
$$C_{eq} = \left(\frac{1}{17.3} + \frac{1}{4.5} \right)^{-1} = 3.57 \text{ MF}$$



V_{AB} have
 V_{AC} none

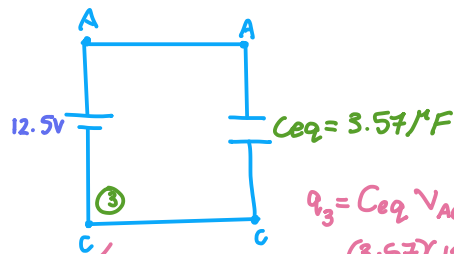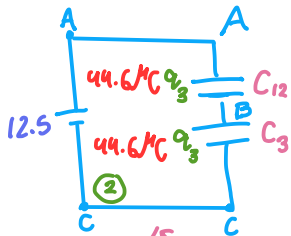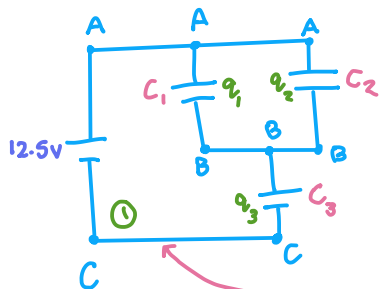

$$C_{12} = 17.3 \mu\text{F}$$

$$C_{eq} = 3.57 \mu\text{F}$$

$$q_1 = C_1 V_{AB} = (12 \mu\text{F}) 2.6 = 31.2 \mu\text{C}$$

$$q_2 = C_2 V_{AB} = (5.3)(2.6) = 13.4 \mu\text{C}$$

$$V_{BC} = \frac{q_3}{C_3} = \frac{44.6 \mu\text{C}}{4.5 \mu\text{F}} = 9.91 \text{V}$$

Two ways:

$$\textcircled{1} V_{AB} = V_{C12} = \frac{q_3}{C_{12}} = \frac{44.6 \mu\text{C}}{17.3 \mu\text{F}} = 2.6 \text{V}$$

$$\textcircled{2} V_{AB} = V_{AC} - V_{BC} = 12.5 - 9.91 = 2.59$$

$$q_3 = C_{eq} V_{AC} \\ (3.57)(12.5) = 44.6 \mu\text{C}$$

Tips:

- Write equation

OR

$$q_2 = q_3 - q_1 = 44.6 - 31.2 = 13.4 \mu\text{C}$$

Tue 10 Feb

Capacitors:

$U = q \cdot V$ Potential difference

energy stored in capacitor

very imp

$$U = \frac{1}{2} q \cdot V$$

$$q = CV$$

$$\textcircled{3} U = \frac{1}{2} CV \cdot V = \frac{1}{2} CV^2$$

$$\textcircled{4} U = \frac{1}{2} q \times \frac{q}{C} = \frac{q^2}{2C}$$


Way of thinking of energy:

Jood is 6
can I compare him with 12 yr old?
No there's no factor that's constant

Recap:

$$C = \frac{\epsilon_0 A}{d}$$

ϵ_0 has units F/m

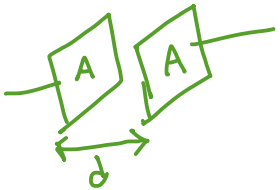

Section 25.4 Energy Stored in an Electric Field

The **electric potential energy** U of a charged capacitor,

$$U = \frac{q^2}{2C} \quad (\text{potential energy}).$$

and

$$U = \frac{1}{2} CV^2 \quad (\text{potential energy}).$$

and

$$U = \frac{1}{2} QV$$

is equal to the work required to charge the capacitor. This energy can be associated with the capacitor's electric field

Energy Stored in an Electric Field

The potential energy of a charged capacitor may be viewed as being stored in the electric field between its plates.

Every electric field, in a capacitor or from any other source, has an associated stored energy. In vacuum, the **energy density** u (potential energy per unit volume) in a field of magnitude E is

$$u = \frac{U}{\text{volume}}$$

$\rightarrow \text{J}$
 $\rightarrow \text{m}^3$

Careful it's not potential difference

$$u = \frac{1}{2} \epsilon_0 E^2 \quad (\text{energy density}).$$

$\rightarrow \text{electric field}$

$\frac{\text{J}}{\text{m}^3}$

Example

- A parallel plate capacitor is fully charged by a 300 V battery. If the area of each plate is 35 cm² and the gap between them is 1.77 mm. What is the charge carried by the capacitor and the energy stored in it?

$$V = 300 \text{ V}$$

$$A = 35 \text{ cm}^2 = 35 \times 10^{-4} \text{ m}^2$$

$$d = 1.77 \text{ mm} = 1.77 \times 10^{-3} \text{ m}$$

$$Q = CV$$

$$\epsilon_0 = 8.85 \times 10^{-12}$$

$$C = \frac{\epsilon_0 A}{d}$$

$$Q = \frac{\epsilon_0 A}{d} (V) = 0.00000000525 \text{ C}$$

$$U = \frac{Q^2}{2C} = \frac{(0.00000000525)^2}{2(1.75 \times 10^{-11})} = \frac{0.0000007875 \text{ J}}{7.9 \times 10^{-7} \text{ J}}$$

Example

IMP

doctor says ab analysis

- A parallel plate capacitor of plate area 82 cm^2 carries a charge of 55 nC when charged at 220 volt . What is the plate separation (d) of this capacitor and the energy stored in it?

$$\begin{aligned}A &= 82 \text{ cm}^2 = 82 \times 10^{-4} \text{ m}^2 \\q &= 55 \text{ nC} = 55 \times 10^{-9} \text{ C} \\V &= 220 \text{ V} \\d &= ?\end{aligned}$$

$$q = CV$$

$$55 \times 10^{-9} = \frac{\epsilon_0 A}{d} (220)$$

$$d = \frac{(8.85 \times 10^{-12})(82 \times 10^{-4})(220)}{55 \times 10^{-9}}$$

$$= 0.00029028 = \boxed{2.9 \times 10^{-4} \text{ m}}$$

$$\begin{aligned}U &= \frac{1}{2} qV \\&= \frac{1}{2} (55 \times 10^{-9})(220)\end{aligned}$$

$$= \boxed{6.05 \times 10^{-6} \text{ J}}$$

Tip
use question
givens

$m \times 10^{-3}$


Example

For the circuit shown, find the voltage, charge and energy stored for each capacitor.


(a) V

(b) q

(c) energy?

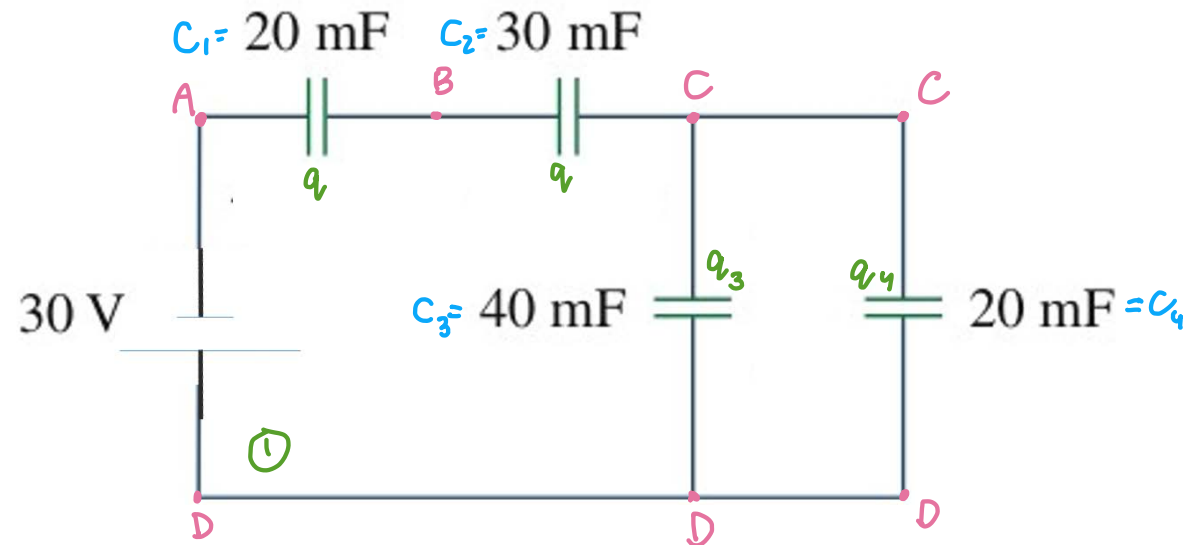


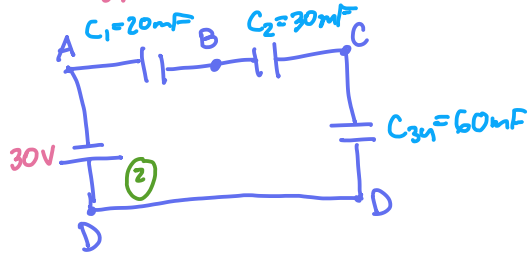C_3 & C_4 parallel:
 $C_{34} = 40 + 20 = 60\text{mF}$



C_1, C_2, C_{34}
are in series
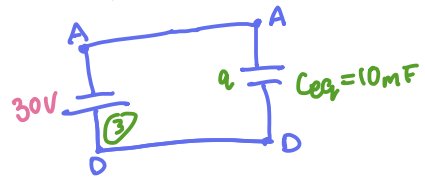
$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_{34}} \right)^{-1} = 10\text{mF}$$



C_{12} & C_{34} series = $C_{eq} = 10\text{mF}$

Thu 5 Feb

Same question continued

Example

- Two capacitors, $C_1 = C$, $C_2 = 2C$, are connected to a battery.
- Which capacitor will store more energy when they are connected to the battery in series? Explain

q is the same

$U = \frac{1}{2}qV$ don't have voltage for all capacitors

$U = \frac{1}{2}CV^2$ eliminated (I'm stupid)

$U = \frac{q^2}{2C}$ ✓ because q doesn't change in series

$$U_1 = \frac{q^2}{2C_1} = \frac{q^2}{2C} \text{ greater}$$

$$U_1 > U_2$$

$$U_2 = \frac{q^2}{2C_2} = \frac{q^2}{2(2C)} = \frac{q^2}{4C}$$

- Which capacitor stores more energy when they are connected in parallel? Explain.

$U = \frac{1}{2}CV^2$ = volt in parallel

$$U_1 = \frac{1}{2}C_1V^2 = \frac{1}{2}CV^2$$

$$U_2 = \frac{1}{2}C_2V^2 = \frac{1}{2} \times 2CV^2 = CV^2 \text{ greater}$$

$$U_1 < U_2$$

Section 25.5 Capacitor with a Dielectric

Definition of a **Dielectric** *insulator between 2 capacitors*

If the space between the plates of a capacitor is completely filled with a **dielectric material**, which is an insulator, the capacitance C in vacuum (or, effectively, in air) is multiplied by the material's **dielectric constant** κ , (Greek kappa) which is a number greater than 1.

In a region completely filled by a dielectric material of dielectric constant κ , all electrostatic equations containing the permittivity constant ϵ_0 are to be modified by replacing ϵ_0 with $\kappa\epsilon_0$.

capacitance even more with an dielectric constant





Copyright ©2022 John Wiley & Sons, Inc. **Figure 25.5.1** The simple electrostatic apparatus used by Faraday. An assembled apparatus (second from left) forms a spherical capacitor consisting of a central brass ball and a concentric brass shell. Faraday placed dielectric materials in the space between the ball and the shell.

Dielectric In a Parallel Plate Capacitor (same charge)

- If a dielectric is placed between the plates of a capacitor it gives a lower potential difference with the same charge, due to the polarization of the material. This increases the capacitance.

Young & Freedman will have opposing

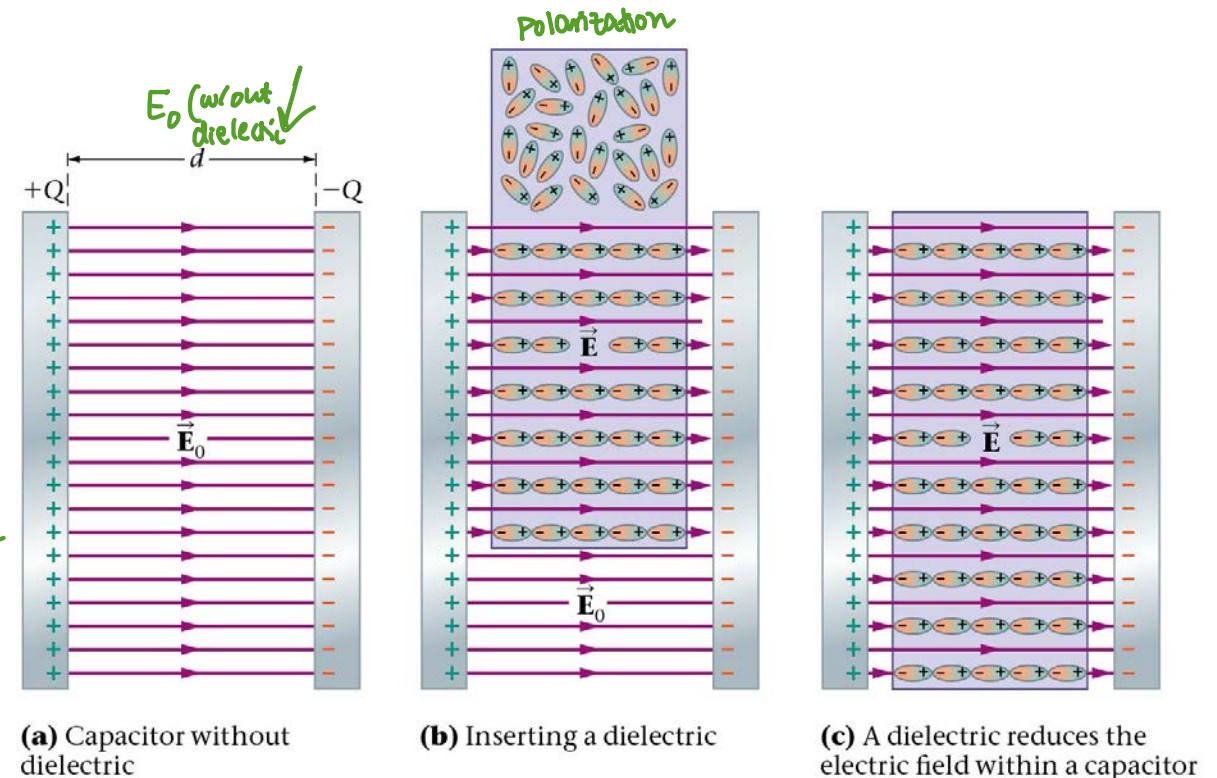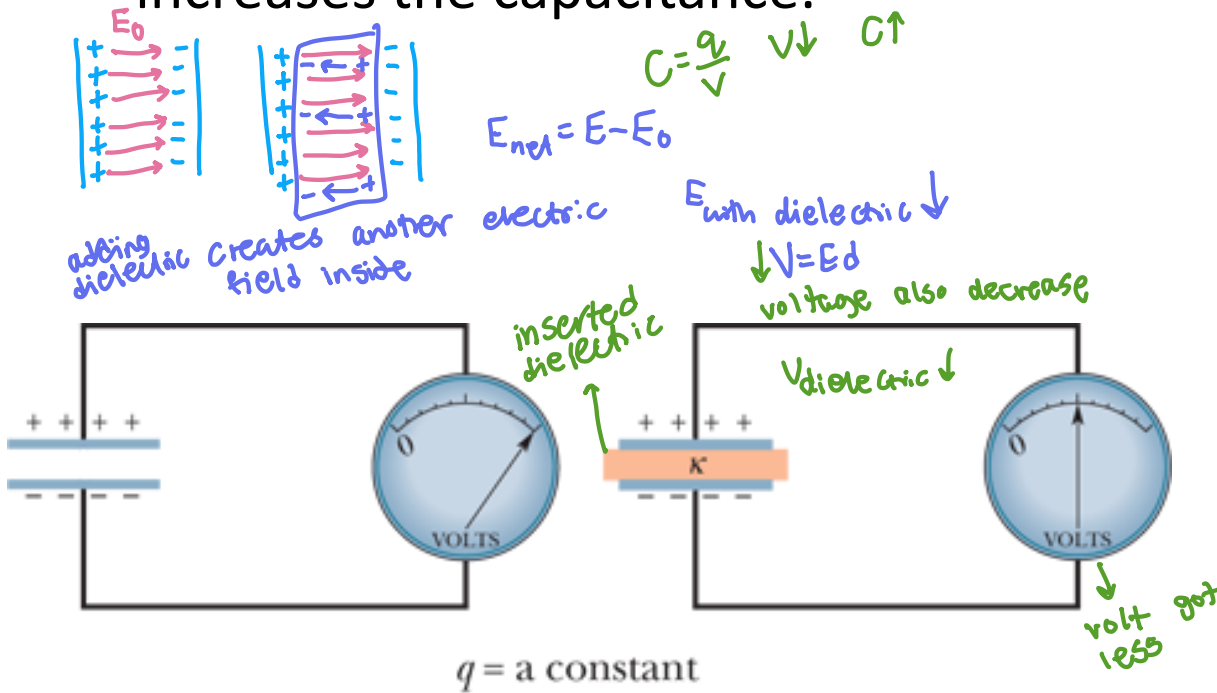

- The polarization of the dielectric results in a lower electric field within it; the new field is given by dividing the original field by the dielectric constant κ :



$$E = \frac{E_0}{\kappa}$$

- Therefore, the capacitance becomes:

$$C = \frac{Q}{V} = \frac{Q}{(V_0/\kappa)} = \kappa \frac{Q}{V_0} = \kappa C_0$$

Ch25

Capacitor

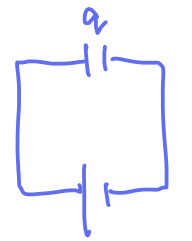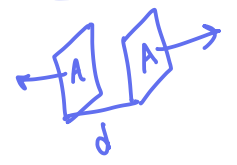

$q = CV$
 $C \leftarrow \downarrow \rightarrow V$
 F

$C = \frac{\epsilon_0 A}{d}$

C series: same charge (q)

$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$



C parallel: same P.d "V"

$C_{eq} = C_1 + C_2 + \dots$

$V = Ed$

Dielectric:

(1) q constant

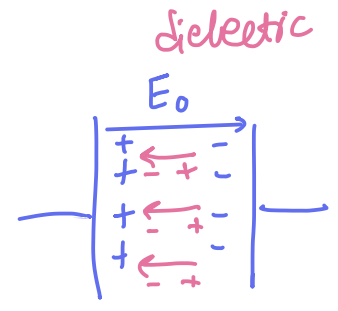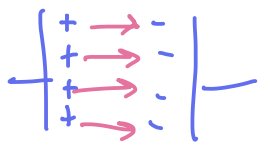

$E_{net} = E_0 - E$ $E = \frac{E_0}{K}$
 $E_{net} \downarrow$

constant
 $q = CV$
 $\uparrow \downarrow$
 $C \uparrow \downarrow V$

$V = Ed$ $E \downarrow$ $V \downarrow$

$\epsilon_0 \equiv K\epsilon_0$
 \downarrow
 dielectric constant

$C = \frac{\epsilon_0 A}{d} = \frac{K\epsilon_0 A}{d}$

- The dielectric constant is a property of the material; here are some examples:

TABLE 20-1 Dielectric Constants

| Substance | Dielectric constant, κ |
|-----------------|-------------------------------|
| Water | 80.4 |
| Neoprene rubber | 6.7 |
| Pyrex glass | 5.6 |
| Mica | 5.4 |
| Paper | 3.7 |
| Mylar | 3.1 |
| Teflon | 2.1 |
| Air | 1.00059 |
| Vacuum | 1 |

Given

usually ← Teflon

- If the electric field in a dielectric becomes too large, it can tear the electrons off the atoms, thereby enabling the material to conduct. This is called **dielectric breakdown**; the field at which this happens is called the dielectric strength.

voltage too high, insulators they can get e⁻ too charged start conducting

TABLE 20-2 Dielectric Strengths

don't forget the minus in previous chapters

| Substance | Dielectric Strength (V / m) |
|-----------------|-----------------------------|
| Mica | 100×10^6 |
| Teflon | 60×10^6 |
| Paper | 16×10^6 |
| Pyrex glass | 14×10^6 |
| Neoprene rubber | 12×10^6 |
| Air | 3.0×10^6 |

(V/m) electric field

Example

- Determine (a) the capacitance and (b) the maximum potential difference that can be applied to a Teflon-filled parallel-plate capacitor having a plate area of 1.75 cm^2 and plate separation of 0.04 mm . (κ for Teflon = 2.1)

$$A = 1.75 \times 10^{-4} \text{ m}^2$$

$$\textcircled{a} \quad C = \frac{\epsilon_0 \kappa A}{d} = \frac{(8.85 \times 10^{-12})(2.1)(1.75 \times 10^{-4})}{0.04 \times 10^{-3}} = 8.13 \times 10^{-11} \text{ F}$$

$$\textcircled{b} \quad \text{Go to table: } 60 \times 10^6 \frac{\text{V}}{\text{m}}$$

$$V = Ed = (60 \times 10^6)(0.04 \times 10^{-3}) = 2.4 \times 10^3 \text{ V}$$

Example

- A parallel-plate capacitor is constructed using a dielectric material whose dielectric constant is 3 and whose dielectric strength is 2×10^8 N/C. The desired capacitance is $0.25 \mu\text{F}$, and the capacitor must withstand a maximum potential difference of 4000 V. Find the minimum area of the capacitor plates.

$$C = 0.25 \times 10^{-6} \text{ F}$$

$$V = 4000 \text{ V}$$


$$K = 3$$

$$A = ?$$

$$V = Ed \rightarrow d = \frac{V}{E} = \frac{4000}{2 \times 10^8} = 2 \times 10^{-5} \text{ m}$$

$$C = \frac{K\epsilon_0 A}{d} \rightarrow \frac{C \cdot d}{K\epsilon_0} = \frac{K\epsilon_0 A}{K\epsilon_0} \rightarrow A = \frac{C \cdot d}{K\epsilon_0} = 1.88 \times 10^{-1} \text{ m}^2$$

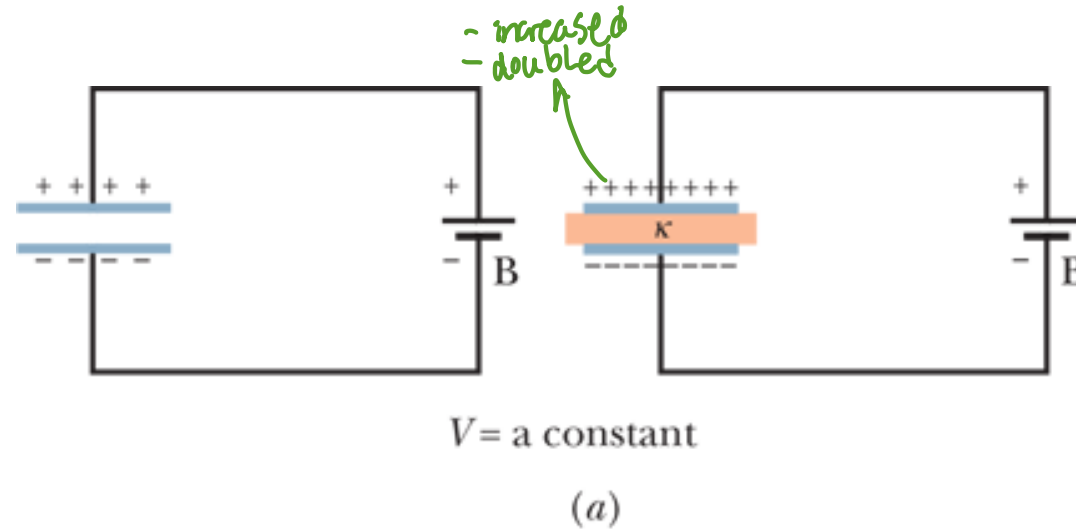Dielectric In a Parallel Plate Capacitor (same potential difference)




Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

If the potential difference between the plates of a capacitor is maintained, as by the presence of battery B, the effect of a dielectric is to increase the charge on the plates.

Extra Practice

q constant
 $U = \frac{1}{2} CV^2$
 $= 1.05 \times 10^{-9} \text{ J}$

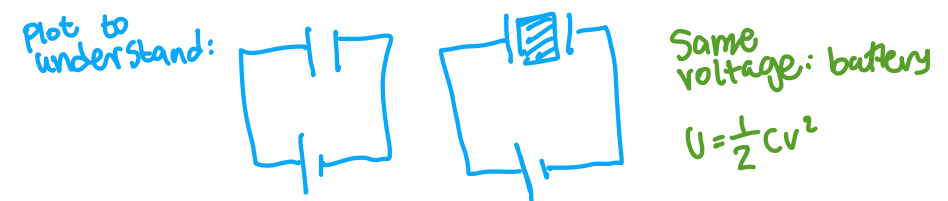$C = 13.5 \times 10^{-12} \text{ F}$
 $V = 12.5 \text{ V}$
 $\kappa = 6.50$



A parallel-plate capacitor whose capacitance C is 13.5 pF is charged by a battery to a potential difference $V = 12.5 \text{ V}$ between its plates. The charging battery is now disconnected, and a porcelain slab ($\kappa = 6.50$) is slipped between the plates.

(a) What is the potential energy of the capacitor before the slab is inserted?

KEY IDEA

We can relate the potential energy U_i of the capacitor to the capacitance C and either the potential V (with [Eq. 25.4.2](#)) or the charge q (with [Eq. 25.4.1](#)):

$$U_i = \frac{1}{2} CV^2 = \frac{q^2}{2C}$$

Calculation: Because we are given the initial potential V ($= 12.5 \text{ V}$), we use [Eq. 25.4.2](#) to find the initial stored energy:

$$U_i = \frac{1}{2} CV^2 = \frac{1}{2} (13.5 \times 10^{-12} \text{ F})(12.5 \text{ V})^2$$

$$= 1.055 \times 10^{-9} \text{ J} = 1055 \text{ pJ} \approx 1100 \text{ pJ. (Answer)}$$

HCS in with graphs

$$U = \frac{q^2}{2\kappa C_0} = \frac{U_i}{\kappa}$$

with dielectric

!! Final exam !!

(b) What is the potential energy of the capacitor-slab device after the slab is inserted?

KEY IDEA

Because the battery has been disconnected, the charge on the capacitor cannot change when the dielectric is inserted. However, the potential *does* change.

Calculations: Thus, we must now use [Eq. 25.4.1](#) to write the final potential energy U_f , but now that the slab is within the capacitor, the capacitance is κC . We then have

$$U_f = \frac{q^2}{2\kappa C} = \frac{U_i}{\kappa} = \frac{1055 \text{ pJ}}{6.50}$$

$$= 162 \text{ pJ} \approx 160 \text{ pJ. (Answer)}$$

When the slab is introduced, the potential energy decreases by a factor of κ .

